

CompArch HW4

Maggie Jakus

October 19, 2017

Deliverable 1

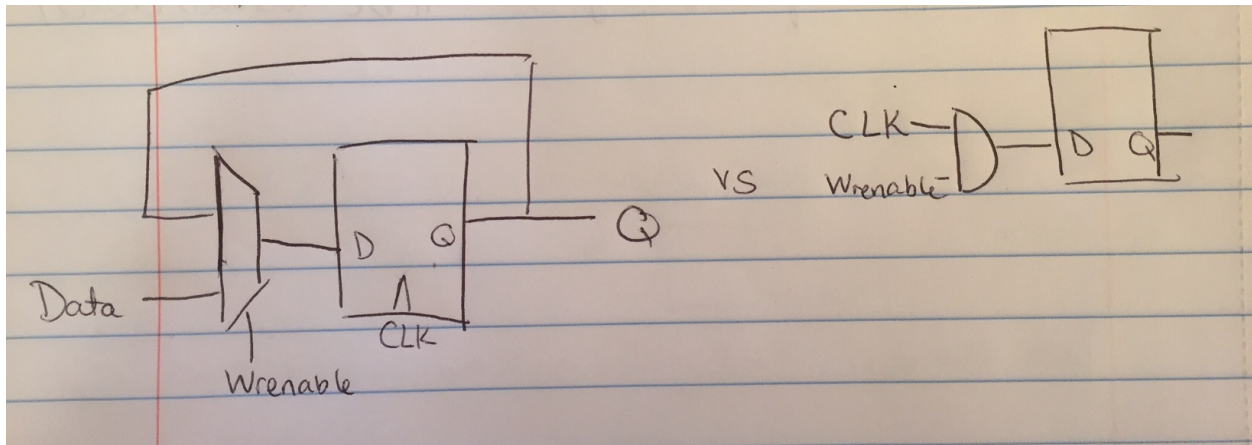


Figure 1

Deliverable 6

The “`jj`” operate denotes “shift x by y , when it is written $x \ll y$. Therefore, when it says “assign out = enable `jj` address”, the enable bit is shifting by the value given by the address (which could be anything from 0 to 31). The enable bit is either 0 (do not write) or 1 (write). If enable is 1, then when it is shifted it will be a 1 at the location that should be written to. This value is then assigned to the output.