
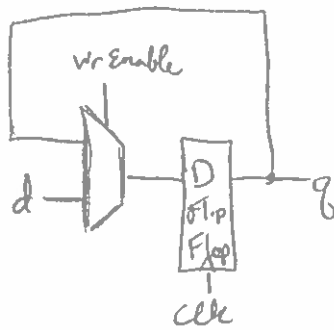


1.

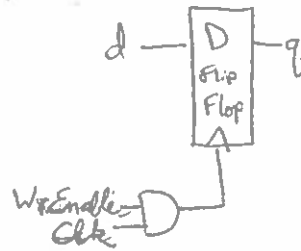

Good



Bad (Glitchy)

6. This module (decoder) shifts the 1 provided by Enable<sup>if high</sup> over address bits, meaning that one & only one of 32 wires is high, with that wire at the corresponding address. These wires can then be used as vrEnables to each register, so that at most only 1 register can be written to.