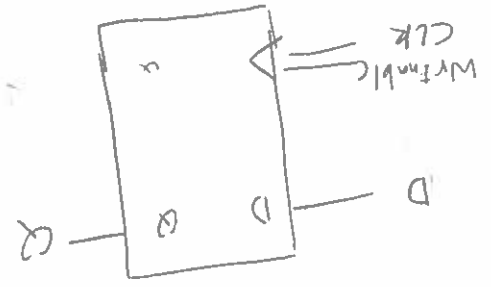



Deliverable 6

The mode will be shift (S) the enable bit by all of the address bit.
 The range will match the output possibilities we can input w/ 5 bits

0.32.



Incorrect Register

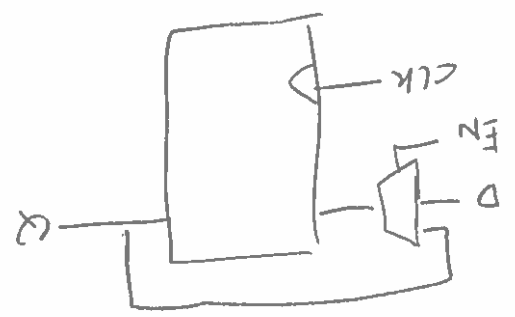

Correct Register

Deliverable 1